

No. of Printed Pages : 4
Roll No.

220933

3rd Sem / Electrical
Subject :Analog & Digital Electronics

Time : 3 Hrs. M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The temperature coefficient of semiconductor is (CO1)

- a) Positive
- b) Zero
- c) negative
- d) None of the above

Q.2 A transistor is a _____ operated device. (CO2)

- a) Current
- b) Voltage
- c) Both current and voltage
- d) None of the above

Q.3 How many diodes does a single-phase Bridge Rectifier consists of? (CO1)

- a) one
- b) two
- c) three
- d) four

(1)

220933

Q.4 A byte is a string of _____ bits. (CO3)

- a) 2
- b) 4
- c) 6
- d) 8

Q.5 A NAND gate is equivalent to an AND gate followed by _____ gate (CO3)

- a) OR
- b) NOT
- c) NOR
- d) AND

Q.6 The number of select line for 8:1 MUX are _____. (CO4)

- a) 6
- b) 4
- c) 2
- d) 3

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 The process of adding impurities is called _____. (CO1)

Q.8 JFET stands for _____ (CO2)

Q.9 Draw symbol of pnp transistor. (CO2)

Q.10 $101001 + 100011 = \text{_____}$. (CO3)

Q.11 The minimum number of flip flops required for a decade counter is _____. (CO4)

Q.12 PISO stands for _____. (CO4)

(2)

220933

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. $(8 \times 4 = 32)$

Q.13 Difference between P and N type semiconductors. $(CO1)$

Q.14 Draw and explain V-I characteristics of a p-n junction diode. $(CO1)$

Q.15 What is need of filter circuit. Explain LC filter circuit. $(CO1)$

Q.16 What is the significance of Ripple factor. $(CO2)$

Q.17 Compare JFET and BJT. $(CO2)$

Q.18 Do the following conversions $(CO3)$

a) $(75)_{10} = (?)_2$

b) $(7B2)_{16} = (?)_8$

Q.19 Explain NOR gate with truth table. $(CO3)$

Q.20 Discuss about Full adder circuit. $(CO4)$

Q.21 Write a short note on 8:1 MUX. $(CO4)$

Q.22 Write a short note on JK FF. $(CO4)$

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. $(2 \times 8 = 16)$

Q.23 Explain in detail full wave bridge rectifier circuit and its advantages and disadvantages. $(CO1)$

Q.24 Explain in detail working of 3 bit synchronous / asynchronous counter. $(CO4)$

Q.25 Write short note on the following .

a) NAND gate as universal gate. $(CO3)$

b) Transistor as an amplifier in CE configuration. $(CO2)$