

## **SECTION-D**

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 Explain any one A/D converter with Suitable Diagram.

Q.24 Discuss construction, operation and characteristics of FET.

Q.25 Describe Counters and their applications with suitable Diagram.

No. of Printed Pages : 4

Roll No. ....

221524

**2nd Sem / Instrumentation & Control Engg.,  
Medical Electronics  
Subject : Analogue and Digital Electronics**

Time : 3 Hrs.

M.M. : 60

## SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 Acceptor type Semiconductors are formed by adding impurity of valances .

Q.2 The most commonly used Transistor circuit arrangement is \_\_\_\_\_.

- a) CE
- b) CB
- c) CC
- d) Both A and B

### Q.3 FET has

- a) High Voltage gain
- b) Large input impedance
- c) Large Power gain
- d) Large output impedance

(240)

(4)

221524

(1)

221524

Q.4 The base value of Hexadecimal No. System is \_\_\_\_\_.

- a) 2
- b) 4
- c) 8
- d) 16

Q.5 An nibble represents \_\_\_\_\_.

- a) 3 bits
- b) 4 bits
- c) 5 bits
- d) 2 bits

Q.6 \_\_\_\_\_ Flip Flop. is used as a latch

- a) T
- b) J-K
- c) Master slave J-K
- d) R S

## SECTION-B

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Expand PISO.

Q.8 Draw Symbol of NAND Gate.

Q.9 Expand JFET.

Q.10 A Transistor has \_\_\_\_\_ terminals.

Q.11 Define Doping.

Q.12 Mention name of any one D/A converter.

## SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 Write a Short note on P and N type semiconductors.

Q.14 Discuss Structure of NPN Transistor.

Q.15 Explain NOR and NAND Gate, with their symbol and truth table.

Q.16 Write short note Note on Sequential Circuits.

Q.17 Compare CB, CE and CC configuration for transistor.

Q.18 Discuss I/P and O/P connections of CE configuration.

Q.19 Explain Diode as a Full wave rectifier.

Q.20 What is Zener Diode and Avalanche break down.

Q.21 Differentiate between MOSFET and BJT.

Q.22 Why NAND Gate is called as a universal Gate.